Digital Design Lab

Ratko Pilipović

2026-11-10

Table of contents

Preface 1

I. Lab Exercises 3

1. First exercise: Tools and the Digital Design Cycle 5
1.1. The digital design cycle 5
1.2. Tools used in this course 6
1.3. Installing Anvil 8
1.4. Your first design: basic_comb 9
1.5. Starter files 13
1.6. Assignment 13

2. Second exercise: Introduction to (System)Verilog 15
2.1. Types 15
2.1.1. Logic (NetList) Types 15
2.1.2. Vector Types 15
2.1.3. Variable Types 15
2.1.4. Expressing Numbers Using Different Bases 16
2.2. Module 16
2.3. Operators 17
2.3.1. Numerical Operators 18
2.3.2. Logical Operators 18
2.3.3. Relational Operators 18
2.3.4. Bitwise Operators 19
2.3.5. Reduction Operators 19

2.3.6. Conditional Operator 20
2.3.7. Concatenation and Replication Operators 20
2.4. Modeling Concurent functionality in SystemVerilog 21
2.4.1. Continuous assignment 21
2.4.2. 4-bit 4:1 Multiplexer 22
2.4.3. 4-bit adder 23
2.4.4. User Constraints Files and Pin Planning in Vivado . 25
2.5. Assignment 26

3. Third exercise: Designing sequential circuits with SystemVerilog 29
3.1. Designing D Flip-Flop in SystemVerilog 29
3.2. Combinational logic with always statement 31
3.3. Common mistakes 33
3.4. Task: Implement a 4-bit Gray Code Counter 35
3.4.1. Example Code Structure: 36
3.5. Implementation guidelines 37
3.5.1. Divider 38
3.5.2. Up/down binary counter 38
3.5.3. Gray code converter 39
3.5.4. Pin mapping 40
3.6. Literature 40

4. Fourth exercise: Structural modeling and Simulation 41
4.1. Parametrized components 43
4.2. Testbenches 45
4.2.1. Simulating with Anvil / Icarus Verilog 49
4.3. Task: Implement a PWM (Pulse-Width Modulation) module for RGB LED 50
4.3.1. PWM time diagram 51
4.3.2. Extension: oscilloscope probe 51
4.4. Implementation guidelines 52
4.4.1. Prescaler 52
4.4.2. PWM controller 53
4.4.3. Top level: rgb_controller 55

4.4.4. Testbenches for prescaler and PWM_controller . . . 58
4.4.5. Pin mapping . . . 63
4.5. Starter files . . . 64

5. Fifth exercise: Counter and seven segment display 65
5.1. Seven segment display . . . 65
5.1.1. Common anode vs common cathode configuration . 65
5.1.2. Nexys A7 and seven-segment display . . . 67
5.2. Assignment . . . 68
5.2.1. Design overview . . . 70
5.2.2. Step 1: Create the project . . . 70
5.2.3. Step 2: `timer_002s` . . . 71
5.2.4. Step 3: `counter_1s` . . . 72
5.2.5. Step 4: `anode_assert` . . . 73
5.2.6. Step 5: `value_to_digit` . . . 74
5.2.7. Step 6: `digit_to_segments` . . . 74
5.2.8. Step 7: `SevSegDisplay` . . . 76
5.2.9. Step 8: `top` . . . 77
5.2.10. Step 9: Simulate . . . 78
5.2.11. Step 10: Pin constraints . . . 79
5.2.12. Step 11: Build and program . . . 80
5.3. Starter files . . . 81

II. Appendix 83

6. Appendix: Using the Oscilloscope and Signal Generator 85
6.1. Equipment . . . 85
6.2. Connecting probes to the FPGA board . . . 86
6.3. Using the Rigol DHO914 oscilloscope . . . 86
6.3.1. Adjusting the display . . . 87
6.3.2. Measuring signal parameters . . . 87
6.4. Using the DG912 Pro signal generator . . . 88

Preface

Every processor, controller, and screen you have ever used began as a handful of logic gates someone arranged on purpose. This book is about learning to do that arranging yourself — not by reading about it, but by designing, simulating, and running your own digital circuits on real hardware.

Over nine labs, you will go from your first combinational circuit to a complete FPGA-based System on Chip: a HIPV, a Risc-V based processor, talking to peripherals you wrote, over a bus you configured, validated with a real oscilloscope. Along the way you will hit the same problems every digital designer hits — a signal that glitches, a counter that free-runs, a testbench that lies to you — and learn to reason your way out of them.

That debugging instinct, more than any single lab, is the point.

Note to Students: These notes are intended solely for educational purposes. They are not a replacement for attending lectures or consulting textbooks, but rather a complementary resource to support your learning.

Part I.

Lab Exercises

1. First exercise: Tools and the Digital Design Cycle

This first lab has two goals. First, to introduce the **digital design cycle** — the sequence of steps every digital circuit goes through, from an idea to a working bitstream on real hardware — so that you understand *why* each later lab does what it does. Second, to get your machine set up with the toolchain we use throughout the course, so the remaining labs are about designing hardware rather than fighting installers.

1.1. The digital design cycle

Every design in this course, however small, passes through the same stages:

1. **Specification** — describe, in plain language, what the circuit must do: its inputs, its outputs, and the relationship between them.
2. **RTL design entry** — write that behavior in a hardware description language. In this course, that language is SystemVerilog.
3. **Functional verification (simulation)** — before touching real hardware, simulate the design against a testbench to check it behaves as specified. Bugs are far cheaper to find here than on a board.
4. **Synthesis** — translate the RTL description into a gate-level netlist: a graph of primitive logic cells and the wires connecting them.

5. **Place & route (implementation)** — map that netlist onto the FPGA's actual resources (logic cells, routing wires, I/O pins), respecting the timing and pin constraints you provide.
6. **Bitstream generation** — package the placed-and-routed design into the binary configuration file the FPGA fabric loads on power-up.
7. **Programming** — load the bitstream onto the physical board.
8. **Hardware validation** — check that the programmed board actually does what you specified in step 1. If it doesn't, you go back to step 1 or 2 and iterate.

Steps 3–7 are exactly what a toolchain automates for you. Knowing this sequence matters because when something goes wrong, the first useful question is *which stage failed* — a syntax error is a design-entry problem, a mismatch with the testbench is a verification problem, an unroutable design is a place & route problem, and an LED that doesn't light despite a clean build is a hardware/pin-constraint problem. Each points you to a different fix.

1.2. Tools used in this course

In previous years this course used **Xilinx Vivado**, a proprietary, vendor-specific design suite. **Starting this year, we use Anvil** — a small, open-source CLI that drives an entirely open FPGA flow (no license, no account, no multi-GB installer). Anvil orchestrates the same stages described above using open tools:

Design cycle stage	Tool
Design entry	SystemVerilog (you write `top.sv`)
Simulation	Icarus Verilog (`iverilog`) + GTKWave, via `anvil test`

Design cycle stage	Tool
Synthesis	`sv2v` (SystemVerilog → Verilog) feeding **Yosys**
Place & route	**VPR** (part of the F4PGA project — Yosys + VPR together)
Bitstream generation	F4PGA
Programming	`openFPGALoader`

Anvil itself just wires these tools together behind a handful of commands (`anvil init`, `anvil build`, `anvil test`, `anvil program`) so you don't invoke each one by hand.

Anvil supports two FPGA boards, the **Digilent Nexys A7 100T** and the **Nexys A7 50T**. Both boards are used across the exercises in this course.

> **i** Nexys A7 50T
>
> Anvil supports both the **Nexys A7 100T** and the **Nexys A7 50T** (support for the 50T was added in Anvil 1.1.0).
> **Your own computer:** a normal installation works out of the box. If you installed Anvil before the 50T was added, run `anvil update` once.
> **Classroom computers:** these have an older Anvil and you cannot run `anvil update` there (it needs `sudo`). Apply the classroom patch instead; it needs no administrator rights and changes only files in your home directory:
>
> ```
> wget https://gist.githubusercontent.com/RatkoFri/d12d34610a58260a58a803eec74e7185/raw/anvi
> bash anvil-nexys50t.sh
> source ~/.bashrc
> ```
>
> Run it once per account; running it again does no harm. Check the

result with `anvil boards` (both boards should be listed) and `anvil doctor`. Then start a 50T project with:

```
anvil init --board Nexys-A7-50T --example switches-leds
```

1.3. Installing Anvil

Prerequisites: a native **Ubuntu 22.04 LTS** machine, or **WSL2** on Windows (the docs call out the handful of WSL-only steps, mainly around forwarding the board's USB connection, as "WSL only"). Docker support is not available yet.

The recommended path is the automated setup script:

```
curl -fsSL https://raw.githubusercontent.com/LogiSmith/toolchain-setup/main/i
```

If you'd rather review the script before running it (always a reasonable instinct when piping a script into a shell):

```
git clone https://github.com/LogiSmith/toolchain-setup.git
cd toolchain-setup
less install.sh
./install.sh
```

A successful run ends with a green `Toolchain installed and all tests passed` banner. Open a **new** shell afterward (so your updated `PATH`/aliases take effect) and verify with:

```
anvil doctor
```

For manual, tool-by-tool installation steps, WSL2-specific USB forwarding, and troubleshooting, see the full LogiSmith installation docs — that page is the canonical reference and is more likely to stay current than a copy pasted here.

> Editor tip: SystemVerilog syntax highlighting and linting in VS Code
>
> Plain `.sv` files have no syntax highlighting in VS Code out of the box. Install Verilog-HDL/SystemVerilog (publisher `mshr-h`) for SystemVerilog syntax highlighting and snippets, plus linting that reports syntax and elaboration errors directly in the editor as you type, instead of only after running `anvil build` or `iverilog`.
> The extension needs to be pointed at a linter. Since this course already installs **Icarus Verilog** as part of the Anvil toolchain, set `verilog.linting.linter` to `iverilog` in the extension's settings rather than installing a separate tool like Verilator or Verible just for this. The `iverilog` executable needs to be on your `PATH`, which the Anvil installer already takes care of.

1.4. Your first design: basic_comb

With `anvil doctor` passing, build a first design that exercises switches and LEDs directly, with no clock involved: a small combinational circuit.

```
mkdir basic_comb && cd basic_comb
anvil init --board Nexys-A7-100T
```

This scaffolds a project:

```
basic_comb/
```

```
config.json     # board + module configuration
top.sv          # top-level design - edit this
*.xdc           # pin constraints, copied from the board master
tb/             # testbenches
Makefile
```

1.4.0.1. What's in `config.json`

`config.json` is the per-project manifest every `anvil` command reads (`build`, `test`, `program`). `anvil init --board Nexys-A7-100T` fills it in for you, so you won't normally hand-edit it in this lab — but it's worth knowing what's there:

```
{
  "project": "basic_comb",
  "board": "Nexys-A7-100T",
  "top": "top",
  "target": "nexys4ddr",
  "partname": "xc7a100tcsg324-1",
  "device": "artix7",
  "ofl_board": "nexys_a7_100",
  "xdc": "Nexys-A7-100T-Master.xdc"
}
```

- **`project`** — the project's name, defaulting to the directory name.
- **`board`** — which entry of Anvil's board registry (`boards.json`) this project targets; everything below `top` is copied in from that registry at `anvil init` time.
- **`top`** — the top-level module name Anvil looks for when it builds your design. It defaults to `top`, which is exactly why the module in `top.sv` needs to be named `top` rather than `basic_comb`.
- **`partname`**, **`device`**, **`target`**, **`ofl_board`**, **`xdc`** — board-specific details (exact FPGA part, device family, Makefile build target,

`openFPGALoader` board identifier, and master constraints filename) that synthesis, place & route, and programming each need. You won't touch these directly for the Nexys A7 100T.

- **`modules`** (not shown above, since this design has none) — a list of reusable RTL module dependencies with pinned versions, e.g. `"uart@1.0.0"`, added automatically by `anvil addmodule`. You'll meet this once a later lab pulls in a shared peripheral block.

Replace the contents of `top.sv` with three switch inputs feeding four LED outputs through simple boolean logic. Anvil expects the top-level module in `top.sv` to be named `top`, so the logic below is the same as the basic_comb.sv starter file, just renamed from `basic_comb` to `top`:

```
// basic_comb - simple 3-input combinational logic
module top (
    input  logic a,        // SW0
    input  logic b,        // SW1
    input  logic c,        // SW2
    output logic [3:0] y   // LED0-LED3
);
    assign y[0] = a & b | c;
    assign y[1] = a & c;
    assign y[2] = a | c;
    assign y[3] = a & b & c;
endmodule
```

1.4.0.2. Explanation

- **Continuous assignment**: each `assign` statement drives its output from a boolean expression of the inputs, re-evaluated any time `a`, `b`, or `c` changes. There is no clock and no memory — the outputs are a pure function of the current switch positions, which is exactly what "combinational logic" means.

- **This is the design-entry stage**: `assign` is the idiomatic way to describe combinational logic in SystemVerilog, the same way `always_ff` (which you'll meet in the next lab) is the idiom for sequential logic.
- **Four independent outputs**: `y[0]`–`y[3]` are four separate circuits sharing the same three inputs — nothing requires a module to have only one output bit.

Uncomment (or check) the pins for `a`, `b`, `c`, and `y` in the generated `.xdc` file — they should look like this:

```
set_property PACKAGE_PIN J15 [get_ports {a}]
set_property IOSTANDARD LVCMOS33 [get_ports {a}]

set_property PACKAGE_PIN L16 [get_ports {b}]
set_property IOSTANDARD LVCMOS33 [get_ports {b}]

set_property PACKAGE_PIN M13 [get_ports {c}]
set_property IOSTANDARD LVCMOS33 [get_ports {c}]

set_property PACKAGE_PIN H17 [get_ports {y[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {y[0]}]

set_property PACKAGE_PIN K15 [get_ports {y[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {y[1]}]

set_property PACKAGE_PIN J13 [get_ports {y[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {y[2]}]

set_property PACKAGE_PIN N14 [get_ports {y[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {y[3]}]
```

This maps `a`, `b`, `c` to switches SW0–SW2 and `y[0]`–`y[3]` to LED0–LED3 on the Nexys A7 100T. Unlike Blinky, there's no `create_clock` line here

— a purely combinational design has no clock port for the timing analyzer to check.

Then build and program the board:

```
anvil build       # sv2v → Yosys → VPR → bitstream, a few seconds
anvil program     # flash the bitstream to the board via openFPGALoader
```

If everything worked, flipping SW0–SW2 should change the LED0–LED3 pattern according to the four equations above.

1.5. Starter files

- basic_comb.sv — the same design used in the walkthrough above, as a ready-to-copy file (module named `basic_comb`; rename to `top` when you copy it into `top.sv`, as noted above).

1.6. Assignment

1. Run `anvil doctor` and confirm every check passes. If something fails, consult the troubleshooting guide before asking for help.
2. Build and program the `basic_comb` design above, and confirm the LED pattern matches the equations for every switch combination.
3. Extend the design with a fifth output, `y[4] = a ^ b ^ c` (XOR of all three switches), wired to LED4. Rebuild, reprogram, and confirm the new output on hardware.

2. Second exercise: Introduction to (System)Verilog

2.1. Types

Commonly used types in SystemVerilog include:

2.1.1. Logic (NetList) Types

- `logic`: A 4-state data type (0, 1, X, Z) used for modeling combinational and sequential logic.
- `bit`: A 2-state data type (0, 1) used for modeling binary data.

2.1.2. Vector Types

- `bit [n-1:0]`: An n-bit unsigned integer.
- `logic [n-1:0]`: An n-bit unsigned integer with 4-state logic.

2.1.3. Variable Types

- `logic`: A 4-state data type (0, 1, X, Z) used for modeling combinational and sequential logic.
- `byte`: An 8-bit signed integer.

- `shortint`: A 16-bit signed integer.
- `int`: A 32-bit signed integer.
- `longint`: A 64-bit signed integer.
- `integer`: A general-purpose 32-bit signed integer (legacy from Verilog).
- `real`: A 64-bit floating point variable.

2.1.4. Expressing Numbers Using Different Bases

```
// Binary representation (base 2)
logic [3:0] binary_num = 4'b1010; // 4-bit binary number 1010 (decimal 10)

// Octal representation (base 8)
logic [5:0] octal_num = 6'o12; // 6-bit octal number 12 (decimal 10)

// Decimal representation (base 10)
logic [7:0] decimal_num = 8'd10; // 8-bit decimal number 10

// Hexadecimal representation (base 16)
logic [7:0] hex_num = 8'hA; // 8-bit hexadecimal number A (decimal 10)
```

2.2. Module

All system modules in Verilog are encapsulated inside a module. Modules can include instantiation of lower-level modules to support hierarchical designs. The keywords `module` and `endmodule` mark the beginning and the end of the system description.

```
module ModuleName(
    portType signalType Port1_name,
    portType signalType Port2_name, Port3_name,
    .......
    portType signalType PortN_name
);
```

where the `portType` specifies the direction of the port (input, output, or inout), and `signalType` defines the type of the signal, as described in the previous section.

Port Type	Description
`input`	Specifies an input port to the module. Data flows into the module through this port.
`output`	Specifies an output port from the module. Data flows out of the module through this port.
`inout`	Specifies a bidirectional port. Data can flow both into and out of the module through this port.

2.3. Operators

SystemVerilog supports a variety of operators that are used for different purposes, including arithmetic, logical, relational, and bitwise operations. Here are some common operators with examples:

2.3.1. Numerical Operators

- `+` : Addition
- `-` : Subtraction
- `*` : Multiplication
- `/` : Division
- `%` : Modulus

```
logic [5:0] c;

// in1 and in2 inputs of module
assign c = in1 + in2;
```

2.3.2. Logical Operators

- `&&` : Logical AND
- `||` : Logical OR
- `!` : Logical NOT

```
logic c;

// in1 and in2 inputs of module
assign c = in1 && in2;
```

2.3.3. Relational Operators

- `==` : Equality
- `!=` : Inequality
- `<` : Less than
- `<=` : Less than or equal to
- `>` : Greater than

- `>=` : Greater than or equal to

```
logic c;

// in1 and in2 inputs of module
assign c
assign c = in1 >= in2;
```

2.3.4. Bitwise Operators

- `&` : Bitwise AND
- `|` : Bitwise OR
- `^` : Bitwise XOR
- `~` : Bitwise NOT
- `<<` : Logical shift left
- `>>` : Logical shift right
- `<<<` : Arithmetic shift left
- `>>>` : Arithmetic shift right

```
logic [5:0] c;

// in1 and in2 inputs of module
assign c = in1 & in2;
```

2.3.5. Reduction Operators

- `&` : Reduction AND
- `|` : Reduction OR
- `^` : Reduction XOR
- `~&` : Reduction NAND
- `~|` : Reduction NOR

- `~^` or `^~` : Reduction XNOR

```
logic [5:0] a;
logic c,d;
assign a = 6'b101010;

// in1 and in2 inputs of module
assign c = &a; // AND reduction result 0
assign d = |a; // OR reduction result 1
```

2.3.6. Conditional Operator

- `? :` : Conditional (ternary) operator

```
logic [5:0] a,b;
logic c;

assign c = (a > b) ? 1'b1 : 1'b0; // cc = either one or zero
```

2.3.7. Concatenation and Replication Operators

The concatenation operator `{}` in SystemVerilog is used to join multiple bits, vectors, or expressions into a single vector.

```
logic [3:0] a = 4'b1010;
logic [3:0] b = 4'b0101;
logic [7:0] c;

// Concatenate a and b to form an 8-bit vector
assign c = {a, b}; // c = 8'b10100101
```

You can also use the replication operator `{n{}}` to replicate a bit or vector `n` times.

```
logic [1:0] d = 2'b11;
logic [5:0] e;

// Replicate d three times to form a 6-bit vector
assign e = {3{d}}; // e = 6'b111111
```

2.4. Modeling Concurent functionality in SystemVerilog

2.4.1. Continuous assignment

Continuous assignment in SystemVerilog allows for the assignment of values to nets using the `assign` keyword, ensuring that the assigned value is continuously updated whenever the right-hand side expression changes. A continuous assignment models combinational logic. For example:

```
assign out = a & b; // 'out' is continuously assigned the result of 'a & b'
```

We need to differ continous assignment from assignment in programming languages.

First example:

```
assign b = a;
assign c = b;
```

In programming languages, a similar construct will first assign the value of `a` to `b`, and then pass the value of `b` to `c`. During synthesis, the tool will remove signal `b` and infer `assign c = a`.

Second example:

```
assign c = a;
assign c = b;
```

In programming languages, a similar construct will first assign the value of `a` to `c`, and then assign the value of `b` to `c`. The final value of `c` will be determined by the last assignment. During synthesis, the tool will create a net driven by two signals. As these signals by have different values, the net `c` will have an unknown value `X`. This situation must be avoided at all costs.

2.4.2. 4-bit 4:1 Multiplexer

The 4-bit multiplexer (MUX) selects one of the four 4-bit inputs to pass to the output based on the 2-bit selection signal.

```
module mux4to1 (
    input logic [3:0] in0, // 4-bit input 0
    input logic [3:0] in1, // 4-bit input 1
    input logic [3:0] in2, // 4-bit input 2
    input logic [3:0] in3, // 4-bit input 3
    input logic [1:0] sel, // 2-bit selection signal
    output logic [3:0] out // 4-bit output
);
    // Nested conditional operator
    // C = (A > B) ? 1 : (A < B) ? 0 : 1
    assign out = (sel == 2'b00) ? in0 :
                 (sel == 2'b01) ? in1 :
```

```
                    (sel == 2'b10) ? in2 :
                    (sel == 2'b11) ? in3 :
                    4'b0000; // Default case

endmodule
```

2.4.2.1. Explanation

- **Module Declaration**: The module `mux4to1` is declared with inputs and outputs.
- **Inputs**: Four 4-bit inputs (`in0`, `in1`, `in2`, `in3`) and a 2-bit selection signal (`sel`).
- **Output**: One 4-bit output (`out`).
- **Conditional Statement**: The `assign` statement uses a series of conditional (ternary) operators to select one of the four inputs based on the value of the 2-bit selection signal (`sel`).

2.4.3. 4-bit adder

The 4-bit adder adds two 4-bit binary numbers and produces a 4-bit sum and a carry-out bit.

```
module adder4bit (
    input logic [3:0] a, // 4-bit input a
    input logic [3:0] b, // 4-bit input b
    output logic [3:0] sum, // 4-bit sum output
    output logic carry_out // Carry-out bit
);

    logic c1, c2, c3; // Intermediate carry bits
```

```
    // Half Adder for the least significant bit
    assign sum[0] = a[0] ^ b[0];
    assign c1 = a[0] & b[0];

    // Full Adder for the second bit
    assign sum[1] = a[1] ^ b[1] ^ c1;
    assign c2 = (a[1] & b[1]) | (c1 & (a[1] ^ b[1]));

    // Full Adder for the third bit
    assign sum[2] = a[2] ^ b[2] ^ c2;
    assign c3 = (a[2] & b[2]) | (c2 & (a[2] ^ b[2]));

    // Full Adder for the most significant bit
    assign sum[3] = a[3] ^ b[3] ^ c3;
    assign carry_out = (a[3] & b[3]) | (c3 & (a[3] ^ b[3]));

endmodule
```

2.4.3.1. Explanation

- **Module Declaration**: The module `adder4bit` is declared with two 4-bit inputs (`a` and `b`), a 4-bit output (`sum`), and a carry-out bit (`carry_out`).
- **Intermediate Carry Bits**: Three intermediate carry bits (`c1`, `c2`, `c3`) are used to store the carry from each adder stage.
- **Half Adder**: The least significant bit is added using a half adder, which produces the sum and the first carry bit (`c1`).
- **Full Adders**: The next three bits are added using full adders, which take into account the carry from the previous stage.
- **Final Carry-Out**: The carry-out from the most significant bit is assigned to `carry_out`.

2.4.4. User Constraints Files and Pin Planning in Vivado

In Vivado, User Constraints Files (UCF) or Xilinx Design Constraints (XDC) files are used to define the physical constraints of the design, such as pin assignments, timing constraints, and other implementation-specific parameters. Pin planning involves mapping the logical signals in your design to the physical pins on the FPGA. This process ensures that the design interfaces correctly with external components and meets the required performance criteria. Proper pin planning and constraint management are crucial for successful FPGA implementation, as they directly impact signal integrity, timing closure, and overall design functionality.

The XDC file for Nexys A7 defines the pin placement for external signals of modules. To map the inputs of our `adder4bit` to the switches and the outputs to LEDs, we need to make the following changes:

```
##Switches
set_property -dict { PACKAGE_PIN J15   IOSTANDARD LVCMOS33 } [get_ports { a[0] }]; #IO_L24N_
set_property -dict { PACKAGE_PIN L16   IOSTANDARD LVCMOS33 } [get_ports { a[1] }]; #IO_L3N_T
set_property -dict { PACKAGE_PIN M13   IOSTANDARD LVCMOS33 } [get_ports { a[2] }]; #IO_L6N_T
set_property -dict { PACKAGE_PIN R15   IOSTANDARD LVCMOS33 } [get_ports { a[3] }]; #IO_L13N_
set_property -dict { PACKAGE_PIN R17   IOSTANDARD LVCMOS33 } [get_ports { b[0] }]; #IO_L12N_
set_property -dict { PACKAGE_PIN T18   IOSTANDARD LVCMOS33 } [get_ports { b[1] }]; #IO_L7N_T
set_property -dict { PACKAGE_PIN U18   IOSTANDARD LVCMOS33 } [get_ports { b[2] }]; #IO_L17N_
set_property -dict { PACKAGE_PIN R13   IOSTANDARD LVCMOS33 } [get_ports { b[3] }]; #IO_L5N_T

##LEDS
## LEDs
set_property -dict { PACKAGE_PIN H17   IOSTANDARD LVCMOS33 } [get_ports { sum[0] }]; #IO_L18
set_property -dict { PACKAGE_PIN K15   IOSTANDARD LVCMOS33 } [get_ports { sum[1] }]; #IO_L24
set_property -dict { PACKAGE_PIN J13   IOSTANDARD LVCMOS33 } [get_ports { sum[2] }]; #IO_L17
set_property -dict { PACKAGE_PIN N14   IOSTANDARD LVCMOS33 } [get_ports { sum[3] }]; #IO_L8P
set_property -dict { PACKAGE_PIN R18   IOSTANDARD LVCMOS33 } [get_ports { carry_out }]; #IO_
```

It is important to assign the appropriate pin to the `get_ports` function.

2.5. Assignment

Your task is to implement a "dummy" 4-bit Arithmetic Logic Unit (ALU) with the following interface: - **a, b**: 4-bit inputs - **alu_control**: 3-bit input for selecting the operation - **c**: 4-bit output

`alu_control` Value	Operation
000	Addition
001	Subtraction
010	Bitwise AND
011	Bitwise OR
100	Bitwise XOR
101	Compare (equal)
110	Pass-through `b`
111	Pass-through `a`

> **Note**
>
> The ALU is 4-bit rather than 6-bit specifically to keep addition/subtraction small. The open-source Artix-7 flow (F4PGA: Yosys + VPR) that Anvil uses has known weak spots mapping inferred carry-chain arithmetic (`+`/`-`) — the same `CARRY4` logic behind the `adder4bit` example above — and wider inferred adders can blow up synthesis time and resource usage. Staying at 4 bits, matching `adder4bit`'s width, keeps you well clear of that.

Tips: 1. Employ operators and intermediate signals to obtain the results of each operation. 2. Connect input signals to the rightmost switches (SW0 to SW7), and selection signals to the leftmost switches (SW13 to

SW15). The output signal should be connected to LEDs (LED0 to LED3).
3. Employ nested conditionals.

3. Third exercise: Designing sequential circuits with SystemVerilog

Vivado recognizes certain idioms and transforms them into specific sequential circuits. Other coding styles may simulate correctly but may synthesize into circuits with obvious or subtle errors. We will present the proper idioms to describe registers and latches.

3.1. Designing D Flip-Flop in SystemVerilog

The Verilog code for a D flip-flop (DFF) active on the positive clock edge with a synchronous reset is given below:

```
module DFF (
    input logic clk,
    input logic reset,
    input logic d,
    output logic q
);
    always_ff @(posedge clk) begin
        if (reset)
            q <= 1'b0;
        else
            q <= d;
```

```
    end
endmodule
```

The `always_ff` has it roots from Verilog language. In Verilog we have `always` statement, written in form:

```
always @(sensitivity_list)
    statement;
```

In the previous code, the statement is executed only when the event specified in the sensitivity list occurs. For the D-FF example, the event is `posedge clk`, meaning the statements inside `always_ff` will execute on the positive edge of the clock. Inside the `always_ff` block, we use an `if/else` statement for conditional operations. Notice that the non-blocking operator `<=` is used inside the `always_ff` block. On every positive edge of the clock, the block checks if the reset is active. If the reset is active, the output will be set to zero; otherwise, the input will be copied to the output. The `always_ff` construct behaves like the `always` construct but is specifically used to imply flip-flops and allows tools to produce a warning if anything else is implied.

Let us design 4-bit counter, which counts on positive edge and has active high reset

```
module Counter4Bit (
    input logic clk,
    input logic reset,
    output logic [3:0] out
);
    logic [3:0] counter;

    always_ff @(posedge clk) begin
        if (reset)
```

```
            counter <= 4'b0000;
        else
            counter <= counter + 1;
    end

    assign out = counter;
endmodule
```

As in the previous example, every time `posedge clk` occurs, the counter will increment the value of the internal counter `counter` if `reset` is low. Otherwise, the counter will start counting from zero. Finally, we output the state of the internal counter to the output. Note that `assign` and `always_ff` work in parallel.

3.2. Combinational logic with always statement

We can design the combinational logic using `always` constructs. Let us first describe an inverter using `always` constructs.

```
module Inverter (
    input logic a,
    output logic y
);
    always_comb begin
        y = ~a;
    end
endmodule
```

In this example, the `always_comb` block is used to describe combinational logic. The output `y` is always the logical NOT of the input `a`. The

`always_comb` construct ensures that the block is always executed whenever any of its inputs change, making it suitable for combinational logic. In the inverter code we use the blocking operator `=`.

> **Note:**
>
> In SystemVerilog, a group blocking assignments (`=`) are evaluated in order they appear. They are used for combinational logic. Non-blocking assignments (`<=`) are used in sequential logic. A group of non-blocking statements is evaluated concurently.

Let us construct 4-to-1 MUX using `always_comb` and `case` construct

```
module Mux4to1 (
    input logic [1:0] sel,
    input logic [3:0] d,
    output logic y
);
    always_comb begin
        case (sel)
            2'b00: y = d[0];
            2'b01: y = d[1];
            2'b10: y = d[2];
            2'b11: y = d[3];
            default: y = 1'b0;
        endcase
    end
endmodule
```

In this example, the `always_comb` block is used to describe the combinational logic for a 4-to-1 multiplexer. The `case` statement selects one of the four input bits `d` based on the 2-bit selector `sel` and assigns it to the

output `y`. The `default` case ensures that `y` is set to `0` if `sel` has an unexpected value. Be sure to always give `default` option in the `case` construct, otherwise you will infer a latch in your design.

3.3. Common mistakes

1. There is no assign construct in always block:

```
module WrongModule1 (
    input logic a,
    input logic b,
    output logic c
);
    always_comb begin
        assign c = a & b;
    end
endmodule
```

2. Having multiple blocks driving the same net

```
module WrongModule2
    ....
    always_ff(@posedge clock) begin
        ......
        c <= {x,1'b0};
    end
    ....
    always_comb begin
        ......
        c = x;
    end
    ....
```

```
    assign c = in1 + in2;
endmodule
```

3. Infering latch in combinational design:

```
logic result;
logic status;

always_comb begin
    if (input_button) begin
        status = 1'b1;
        result = 1'b0;
    end
    else if (done_signal) begin
            status = 1'b0;
        end
    end
```

What is the value of `result` when `done_signal` is high? What will happen when `input_button` and `done_signal` are low? The hardware synthesizer will assume the old value, thereby inferring a latch. You do not want a latch in a combinational design.

Correct answer would be:

```
logic result;
logic status;

always_comb begin
    if (input_button) begin
        status = 1'b1;
        result = 1'b0;
    end
    else if (done_signal) begin
```

```
            status = 1'b1;
            result = 1'b0;
        end
        else begin
            status = 1'b0;
            result = 1'b0;
        end
    end
```

Remember cover all your cases!

3.4. Task: Implement a 4-bit Gray Code Counter

Your task is to implement a 4-bit Gray Code counter, that changes its state with the frequency of 1 Hz.

Steps required: 1. Start with two counters: a modulo 100*10^6 counter and a classical binary counter that counts from 0 to 15. 2. The first counter increments its value every system clock cycle. 3. The other counter changes its value when the first counter reaches the value 100*10^6-1. When the input *up_down* is equal to 0, the counter increments its value; otherwise it decreases. 4. Convert the state of the binary counter to Gray Code.

Python code snippet that illustrates the behaviour of gray code counter

```
binary_count = 0;

while(1):
    for i in range (0, 100 * 1e6): # the module 100*1e6 counter
        if(i==100 * 1e6-1):
            if(up_down==0):
                binary_count = binary_count + 1
```

```
            else:
                binary_count = binary_count - 1

    gray_code = bin2gray(binary_count )
```

```
def bin2gray(binary):
    match binary:
        case 0: return 0
        case 1: return 1
        case 2: return 3
        case 3: return 2
        case 4: return 6
        case 5: return 7
        case 6: return 5
        case 7: return 4
        case 8: return 12
        case 9: return 13
        case 10: return 15
        case 11: return 14
        case 12: return 10
        case 13: return 11
        case 14: return 9
        case 15: return 8
        case _: return 0
```

3.4.1. Example Code Structure:

```
module gray_code_counter (
    input logic clk,
    input logic rst, // Button
    input logic up_down, // Switch for up/down counting
```

```
    output logic [3:0] gray_code // connect the output to LEDs
);

    logic en;
    logic [3:0] binary_count;

    // Prescaler code & binary counter


    // Gray Code Converter
    // employ always_comb and case statement
    // to convert from code to another

endmodule
```

Tip: Binary to graycode converter

3.5. Implementation guidelines

Structural modeling, splitting a design into separate modules and instantiating them, is introduced in the next exercise. For now `gray_code_counter` stays a single module, so the three pieces below are not separate modules with their own ports, but three cooperating pieces of behavioral code inside `gray_code_counter`, sharing the internal signals `en` and `binary_count` already declared in the skeleton above. These three pieces of code are actually three separate `always` blocks, where first two are `always_ff` and the last one is `always_comb`. The first two blocks are sequential, the last one is combinational. The three pieces are described below.

3.5.1. Divider

The divider turns the 100 MHz system clock into a single, once-per-second pulse on `en`. It is a free running counter, the same idea you will meet again as the standalone `prescaler` module in the next exercise.

Declare an internal register wide enough to count up to 100,000,000:

```
logic [26:0] div_count; // 2^27 > 100,000,000
```

Behavior:

- On every rising edge of `clk`, if `rst` is high, reset `div_count` to zero.
- Otherwise, increment `div_count` by one on every rising edge. This is step 2 from above, the first counter incrementing every system clock cycle.
- When `div_count` reaches 100,000,000 - 1, drive `en` high for that clock cycle and let `div_count` wrap back to zero on the next edge, restarting the count.
- The result is a single clock cycle pulse on `en` once every 100,000,000 clock cycles. At 100 MHz that is exactly once per second.

3.5.2. Up/down binary counter

`binary_count` is the 4-bit counter whose value eventually gets Gray encoded for the LEDs. Unlike `div_count`, it does not advance on every clock edge. It only advances once per second, on a clock edge where `en` is high.

Behavior:

- On every rising edge of `clk`, if `rst` is high, reset `binary_count` to zero.

- Otherwise, only change `binary_count` on a clock edge where `en` is high. When `up_down` is 0, increment `binary_count`, wrapping from 15 back to 0. When `up_down` is 1, decrement it, wrapping from 0 back to 15.
- On a clock edge where `en` is low, hold `binary_count` at its current value.
- Because `en` pulses only once per second, `binary_count` also only changes once per second, which is where the counter's 1 Hz update rate comes from.

3.5.3. Gray code converter

The converter has no state of its own. It is a purely combinational function of `binary_count`, mapping each of the 16 possible values to the corresponding Gray code word from the `bin2gray` table above.

Behavior:

- Use `always_comb` with a `case` statement on `binary_count`, one branch per value 0 through 15, assigning the matching Gray code word to `gray_code` in each branch.
- Always include a `default` branch, even though cases 0 through 15 already cover every possible 4-bit value. The Common mistakes section earlier in this chapter explains why an incomplete `case` without a `default` infers a latch instead of the combinational logic you intended.
- Because the conversion is combinational, `gray_code` updates immediately whenever `binary_count` changes. No separate clocking is needed here. `binary_count` already only changes once per second, so `gray_code` will too.

3.5.4. Pin mapping

Connect the `clk` signal to the system clock (100 MHz), the `rst` signal to the middle button, the `up_down` signal to the switch, and the `gray_code` signal to the LEDs.

```
## Clock signal
set_property -dict { PACKAGE_PIN E3    IOSTANDARD LVCMOS33 } [get_ports { cl
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports


##Switches
set_property -dict { PACKAGE_PIN J15   IOSTANDARD LVCMOS33 } [get_ports { up_

## LEDs
set_property -dict { PACKAGE_PIN H17   IOSTANDARD LVCMOS33 } [get_ports { gra
set_property -dict { PACKAGE_PIN K15   IOSTANDARD LVCMOS33 } [get_ports { gra
set_property -dict { PACKAGE_PIN J13   IOSTANDARD LVCMOS33 } [get_ports { gra
set_property -dict { PACKAGE_PIN N14   IOSTANDARD LVCMOS33 } [get_ports { gra

##Buttons
set_property -dict { PACKAGE_PIN N17   IOSTANDARD LVCMOS33 } [get_ports { rst
```

3.6. Literature

1. UC Davis Notes, Verilog: Common mistakes

4. Fourth exercise: Structural modeling and Simulation

In the previous exercise, we focused on designing counters or flip-flops by describing their functionality in SystemVerilog. This style of modeling is referred to as behavioral modeling. This exercise focuses on structural modeling, where we describe a module in terms of how it is composed of simpler modules. In the example below, we assemble a 4:1 multiplexer from three 2:1 multiplexers. Each copy of the 2:1 multiplexer is called an instance and has a unique name.

```
module mux2to1 (
    input logic a,
    input logic b,
    input logic sel,
    output logic y
);
    assign y = sel ? b : a;
endmodule

module mux4to1 (
    input logic [3:0] d,
    input logic [1:0] sel,
    output logic y
);
    logic y0, y1;
```

```
    // instance mux_low of module mux2to1
    mux2to1 mux_low (
        .a(d[0]),
        .b(d[1]),
        .sel(sel[0]),
        .y(y0)
    );

    // instance mux_high of module mux2to1
    mux2to1 mux_high (
        .a(d[2]),
        .b(d[3]),
        .sel(sel[0]),
        .y(y1)
    );

    // instance mux_final of module mux2to1
    mux2to1 mux_final (
        .a(y0),
        .b(y1),
        .sel(sel[1]),
        .y(y)
    );
endmodule
```

As we can see, the instantiation of a module has following syntax: first, we specify the module name, followed by the instance name. In parentheses, we connect the module's inputs and outputs to signals defined at the current level of hierarchy.

```
// module name - mux2to1
// instance name - mux_final
// parenthesis - we map ports
```

```
//              - .a(y0) - port a of module is connected to signal y0
mux2to1 mux_final (
        .a(y0),
        .b(y1),
        .sel(sel[1]),
        .y(y)
    );
// alternative, more C-like instation
// mux2to1 mux_final(y0,y1,sel[1],y)
```

The bellow image depicts the resulting design:

4.1. Parametrized components

So far, all of our modules have had fixed-width inputs and outputs. SystemVerilog allows variable-width modules through the use of parameterized modules. The code below illustrates a parameterized counter module with a variable length output signal.

```
module counter #(
    // Default value if we do ommit
    // WIDTH parameter while instatiating module
    parameter WIDTH = 8
) (
    input logic clk,
    input logic reset,
    output logic [WIDTH-1:0] count
);
    logic [WIDTH-1:0] count_reg;

    always_ff @(posedge clk) begin
```

```
        if (reset) begin
            count_reg <= 0;
        end else begin
            count_reg <= count_reg + 1;
        end
    end

    assign count = count_reg;
endmodule
```

This module defines a counter with a parameterized width. To instatiate in a another module, we need to do following:

```
module top(
    input logic clk,
    input logic reset,
    input logic [15:0] count);

    // Instantiate the counter with a width of 16
    counter #(
        .WIDTH(16)
    ) counter_inst (
        .clk(clk),
        .reset(reset),
        .count(count)
    );
endmodule
```

To define parameters inside a module, we can use local parameters (`localparam`). Verilog HDL local parameters are identical to parameters except that they cannot be directly modified by `defparam` statements or module instance parameter value assignments.

```
    ....
    localparam CNT_WIDTH = 16;

    // Instantiate the counter with a width of 16
    counter #(
        .WIDTH(CNT_WIDTH)
    ....
```

4.2. Testbenches

A testbench is an HDL module used to test another module, known as the device under test (DUT) or unit under test (UUT). The testbench includes statements to apply inputs to the DUT and, ideally, to verify that the correct outputs are generated. The input and expected output patterns are referred to as test vectors.

Let us write the DUT for our 4:1 MUX. Lets fix length to 4-bit.

```
module tb_mux4to1;

    // Testbench signals
    logic [3:0] d;
    logic [1:0] sel;
    logic y;

    // Instantiate the DUT
    mux4to1 dut (
        .d(d),
        .sel(sel),
        .y(y)
    );

    // Test procedure
```

```
    initial begin
        // Test case 1
        // Define values for inputs
        d = 4'b1010; sel = 2'b00;
        // Wait for 10 time units
        #10;
        // print on STD
        $display("d=%b sel=%b y=%b", d, sel, y);

        // Test case 2
        d = 4'b1010; sel = 2'b01;
        #10;
        $display("d=%b sel=%b y=%b", d, sel, y);

        // Test case 3
        d = 4'b1010; sel = 2'b10;
        #10;
        $display("d=%b sel=%b y=%b", d, sel, y);

        // Test case 4
        d = 4'b1010; sel = 2'b11;
        #10;
        $display("d=%b sel=%b y=%b", d, sel, y);

        // Finish simulation
        $finish;
    end
endmodule
```

A testbench has no ports of its own. It sits at the top of the simulation hierarchy, so everything it needs (`d`, `sel`, `y`) is declared as a plain `logic` signal inside the module and then wired to the DUT by name, exactly as you would wire a module instance in any other design. `mux4to1` is purely

combinational, so the testbench doesn't need to worry about clocking it at all. The `initial` block simply drives a new value onto `d`/`sel`, waits `#10` time units for the change to propagate through the DUT's `assign` statements, and then `$display`s the result. The `#10` delay here isn't required by the circuit, since a combinational output settles essentially instantly. It just gives each test case a clean slice of simulation time so the four `$display` lines don't collide, and makes the resulting waveform easier to read if you open it in GTKWave. Each of the four test cases holds `sel` at all four possible values while `d` stays fixed, letting you check by eye that `y` always equals the bit of `d` selected by `sel`. `$finish` at the end tells the simulator to stop. Without it, a testbench with no more statements to execute would simply hang.

For testing sequential design, we need to account the clock signal. In testbenches we need to create a separate always block that will generate clock signal. Bellow code shows the testbench for our parametrized counter (case for 4-bit).

```
module tb_counter;

    // Testbench signals
    logic clk;
    logic reset;
    logic [3:0] count;

    // Instantiate the DUT
    counter #(
        .WIDTH(4)
    ) dut (
        .clk(clk),
        .reset(reset),
        .count(count)
    );
```

```
    // Clock generation
    always begin
        #5 clk = ~clk; // Toggle clock every 5 time units
    end

    // Test procedure
    initial begin
        // Initialize signals
        clk = 0;
        reset = 1;
        // Apply reset
        #10;
        reset = 0;
        // Wait for some time and observe the count
        #100;
        $display("count=%b", count);
        // Finish simulation
        $finish;
    end
endmodule
```

Unlike the MUX testbench, `counter` is a registered design (`always_ff`), so its output only changes on a rising `clk` edge. The testbench has to actually supply that clock, since nothing else in simulation will. That's what the separate `always` block does. With no sensitivity list and no guarding `if`, it just keeps re-executing `#5 clk = ~clk;` for the entire simulation, flipping `clk` every 5 time units and producing a free-running clock with a 10-unit period. This block runs concurrently with the `initial` block below it. In SystemVerilog, every `initial`/`always` block in a module starts at time 0 and proceeds independently, which is exactly why the clock generator has to live in its own block rather than inside the stimulus sequence.

The `initial` block still drives the test, but now in terms of clock edges rather than raw delays. It sets `clk = 0` and `reset = 1` at time 0, holds

`reset` high for `#10` (one full clock period) to model a real power-on reset pulse, then deasserts it and waits `#100` (ten clock periods) for the counter to free-run before sampling `count` with `$display`. That wait is the key difference from the combinational case. A combinational output is valid almost immediately after its inputs change, but a register only updates once per clock edge, so a sequential testbench must always budget enough simulated time (or, in more thorough testbenches, wait for a specific number of `@(posedge clk)` events) before checking the DUT's outputs. `$finish` matters more here than in the MUX testbench, because the clock-generation `always` block never terminates on its own. Without an explicit `$finish`, the simulation would run forever.

4.2.1. Simulating with Anvil / Icarus Verilog

Save the testbench alongside the DUT it exercises. Inside an Anvil project, place it under `tb/` and let `anvil test` drive Icarus Verilog for you:

```
anvil test tb/tb_mux4to1.sv     # runs Icarus Verilog, writes tb/tb_mux4to1.vcd
```

You can also invoke Icarus Verilog directly. This is handy while experimenting with standalone snippets like the ones above, outside of a full Anvil project. `iverilog` compiles every file passed on the command line into a single simulation executable, which `vvp` then runs:

```
iverilog -g2012 -o sim mux2to1.sv mux4to1.sv tb_mux4to1.sv
vvp sim
```

`-g2012` selects SystemVerilog-2012 syntax, needed for constructs like `logic` and `always_ff` that plain Verilog doesn't have. The `$display` calls in the testbench print straight to the terminal.

To inspect signals over time instead of just the printed values, add a dump block to the testbench:

```
initial begin
    $dumpfile("tb_counter.vcd");
    $dumpvars(0, tb_counter);
end
```

then open the resulting `.vcd` file in GTKWave:

```
gtkwave tb_counter.vcd &
```

4.3. Task: Implement a PWM (Pulse-Width Modulation) module for RGB LED

In this task, you will implement a PWM module for an RGB LED. The module will have three 6-bit inputs, each controlling the duty cycle of the red, green, and blue LEDs. The module will have three 1-bit outputs, each representing the PWM signal for the red, green, and blue LEDs.

The PWM signal will be generated by comparing the duty cycle with a 4-bit counter that increments with the PWM_tick signal. The PWM_tick signal is generated by a prescaler that outputs a pulse every 3125 clock cycles, corresponding to a frequency of 32 kHz. You will connect the PWM module to the prescaler and the RGB LED module according to the diagram below.

> Note: The N16, R11, and G14 pins on the FPGA board are connected to the red, green, and blue LEDs of the RGB LED, respectively.

Switch values denote duty cycle for each color. The duty cycle is calculated as follows:

SW[1:0]	Duty_cycle
00	0 %
01	12.5 %
10	25 %
11	50 %

Duty cycle is definied as ratio of high signal to the period of the signal, e.g. 25% duty cycle means that the signal is high for 25% of the period.

4.3.1. PWM time diagram

4.3.2. Extension: oscilloscope probe

An LED only tells you the PWM signal's average brightness. To actually see the waveform, duty cycle, and period on an oscilloscope, add two more switches, `SW[7:6]`, that select which of the three RGB PWM signals gets mirrored onto a new single-bit output port, `pwm_out`. Wire `pwm_out` to a Pmod header pin so you can clip a scope probe onto it. For connecting the probe and reading the signal once it's wired up, see the oscilloscope appendix.

`SW[7:6]`	`pwm_out` drives
00	`RGB[0]` (red)
01	`RGB[1]` (green)
10	`RGB[2]` (blue)
11	`1'b0`

4.4. Implementation guidelines

4.4.1. Prescaler

The prescaler turns the fast system clock into the slower `pwm_tick` the PWM module counts on. It is a free running counter that produces a single cycle pulse once every `limit` clock cycles. Its interface is already declared in the starter file:

```
module prescaler
    #(parameter PRESCALER_WIDTH = 8)
    (
        input logic clk,
        input logic rst,
        input logic [PRESCALER_WIDTH-1:0] limit,
        output logic pwm_tick
    );
```

Port	Direction	Width	Description
`clk`	input	1 bit	System clock. The counter advances on its rising edge.
`rst`	input	1 bit	Synchronous reset. Clears the internal counter while high.
`limit`	input	`PRESCALER_WIDTH` bits	Number of clock cycles between output pulses.

Port	Direction	Width	Description
`pwm_tick`	output	1 bit	Pulses high for one clock cycle, once every `limit` cycles.

Behavior:

- Keep an internal counter register. On every rising edge of `clk`, if `rst` is high, reset that counter to zero.
- Otherwise, increment the counter by one on every rising edge.
- When the counter reaches `limit - 1`, drive `pwm_tick` high for that clock cycle and let the counter wrap back to zero on the next edge, restarting the count.
- The result is a periodic, single cycle pulse with a period of exactly `limit` clock cycles. With `limit = 3125` and a 100 MHz `clk`, `pwm_tick` fires once every 31.25 microseconds, which is 32 kHz.

4.4.2. PWM controller

The PWM controller turns a 2-bit duty cycle selection into a single PWM output for one LED color. One instance drives the red LED, one drives green, one drives blue, each fed by its own pair of switches and all three sharing the same `pwm_tick` from the prescaler. Its interface is already declared in the starter file:

```
module PWM_controller
(
    input logic clk,
    input logic rst,
    input logic [1:0] SW,
    input logic pwm_tick,
```

```
    output logic PWM
);
```

Port	Direction	Width	Description
`clk`	input	1 bit	System clock, used to advance the internal counter register.
`rst`	input	1 bit	Synchronous reset. Clears the internal counter while high.
`SW`	input	2 bits	Duty cycle selector for this color, per the duty cycle table above.
`pwm_tick`	input	1 bit	One clock cycle pulse from the prescaler. Acts as a count enable.
`PWM`	output	1 bit	The pulse width modulated signal driving one RGB LED color.

Behavior:

- Keep an internal 4-bit counter register. Unlike the prescaler, this counter does not advance on every `clk` edge. It advances by one

only on a `clk` edge where `pwm_tick` is high, and wraps from 15 back to 0. Sixteen `pwm_tick` pulses therefore make up one full PWM period.

- On a `clk` edge where `rst` is high, reset that counter to zero instead of counting.
- Translate `SW` into a threshold on the same 0 to 15 scale as the counter, so it lines up with the duty cycle table: `00` maps to a threshold of 0, `01` to 2, `10` to 4, and `11` to 8 (0, 2, 4, and 8 sixteenths are 0%, 12.5%, 25%, and 50%).
- Drive `PWM` combinationally from the comparison: high while the counter value is less than the threshold, low otherwise. Since the counter counts through all 16 values once per period, this produces a high pulse whose width, as a fraction of the period, equals the selected duty cycle.

4.4.3. Top level: rgb_controller

The top module has no logic of its own beyond the oscilloscope channel selector described below. It otherwise only wires the prescaler and three `PWM_controller` instances together, using structural modeling exactly as introduced at the start of this chapter. Its interface, extended with the oscilloscope probe from the task above, is already declared in the starter file:

```
module rgb_controller (
    input logic clock,
    input logic reset,
    input logic [7:0] SW,
    output logic [2:0] RGB,
    output logic pwm_out
);
```

Port	Direction	Width	Description
`clock`	input	1 bit	System clock (100 MHz), forwarded to every instance below.
`reset`	input	1 bit	Synchronous reset, forwarded to every instance below.
`SW`	input	8 bits	`SW[5:0]`: duty cycle selectors, two bits per color (`SW[1:0]` red, `SW[3:2]` green, `SW[5:4]` blue). `SW[7:6]`: oscilloscope channel select.
`RGB`	output	3 bits	One PWM signal per color: `RGB[0]` red, `RGB[1]` green, `RGB[2]` blue.
`pwm_out`	output	1 bit	Mirrors whichever `RGB` bit `SW[7:6]` selects, for probing with an oscilloscope.

Structure:

- One instance of `prescaler`, driven by `clock`/`reset` and the `limit_value` already wired up in the draft, produces a single `pwm_tick` signal shared by everything downstream.
- Three instances of `PWM_controller`, conventionally named `PWM_red`, `PWM_green`, and `PWM_blue`. These are three separate instances of the exact same module, the same way `mux2to1` was instantiated three times to build `mux4to1` earlier in this chapter, not three different modules. Each instance shares `clock`, `reset`, and the one `pwm_tick` from the prescaler, but connects to a different 2-bit slice of `SW` and drives a different bit of `RGB`. For example, the red instance looks like:

```
PWM_controller PWM_red (
    .clk(clock),
    .rst(reset),
    .SW(SW[1:0]),
    .pwm_tick(pwm_tick),
    .PWM(RGB[0])
);
```

`PWM_green` and `PWM_blue` follow the same pattern, connecting `SW[3:2]`/`RGB[1]` and `SW[5:4]`/`RGB[2]` respectively. The draft file's instantiation comments all read "for the red LED". That's a leftover from copy-pasting the first instance, and should read green and blue for the other two.

- On top of the three instances above, drive `pwm_out` from `RGB` with a combinational multiplexer on `SW[7:6]`, using `always_comb` and `case` exactly as introduced for `Mux4to1` in the previous exercise:

```
always_comb begin
    case (SW[7:6])
        2'b00: pwm_out = RGB[0];
        2'b01: pwm_out = RGB[1];
```

```
        2'b10: pwm_out = RGB[2];
        default: pwm_out = 1'b0;
    endcase
end
```

`SW[7:6] = 2'b11` has no explicit case, so it falls through to `default`, holding `pwm_out` at `1'b0` rather than leaving it undriven. Always keep that `default` branch, even on cases that look fully covered. Leaving it out, as the "Infering latch" mistake earlier in the previous chapter explains, would infer a latch instead of the combinational multiplexer you want.

- Create a testbench to verify the functionality of your PWM module. The testbench is provided in the repository.

4.4.4. Testbenches for prescaler and PWM_controller

Before wiring everything together, verify `prescaler` and `PWM_controller` on their own, the same way `tb_mux4to1` and `tb_counter` tested individual modules earlier in this chapter. A bug isolated to one small module is far easier to find than the same bug hiding inside the fully assembled `rgb_controller`.

4.4.4.1. tb_prescaler

```
module tb_prescaler;

    // Testbench signals
    logic clk;
    logic rst;
    logic [7:0] limit;
```

```
    logic pwm_tick;

    // Instantiate the DUT
    prescaler dut (
        .clk(clk),
        .rst(rst),
        .limit(limit),
        .pwm_tick(pwm_tick)
    );

    // Clock generation
    always begin
        #5 clk = ~clk; // Toggle clock every 5 time units
    end

    // Test procedure
    initial begin
        $dumpfile("tb_prescaler.vcd");
        $dumpvars(0, tb_prescaler);

        clk = 0;
        rst = 1;
        limit = 5;
        #10;
        rst = 0;

        // Let the counter run through several periods
        #200;

        $finish;
    end

    // Log every pwm_tick pulse
```

```
    always @(posedge clk) begin
        if (pwm_tick)
            $display("t=%0t pwm_tick pulse", $time);
    end

endmodule
```

> **Note**
>
> Do not test with `limit = 3125`, the value you will eventually use on hardware. At 100 MHz that is a pulse every 31.25 microseconds, so watching even a handful of periods in simulation means sitting through thousands of clock cycles of `$display` output or a huge waveform. Drive `limit` with a small value instead, such as 5 as above, so `pwm_tick` fires every few clock cycles and you can see several full periods and the counter wraparound in a short simulation run. Once the counting and wraparound logic is confirmed correct at a small limit, the same logic is correct at `limit = 3125`, only slower.

4.4.4.2. tb_pwm_controller

`PWM_controller` takes `pwm_tick` as an input rather than generating it, so this testbench stands in for the prescaler with a small free running counter of its own, pulsing `pwm_tick` high for one clock cycle out of every 4, instead of instantiating a full `prescaler` with a large `limit`. The DUT's internal counter then advances once every 4 clock cycles, so a full 16-step PWM period takes 64 clock cycles to simulate, still far shorter than testing against the real `limit = 3125` prescaler.

```
module tb_pwm_controller;
```

```
// Testbench signals
logic clk;
logic rst;
logic [1:0] SW;
logic pwm_tick;
logic PWM;

// Instantiate the DUT
PWM_controller dut (
    .clk(clk),
    .rst(rst),
    .SW(SW),
    .pwm_tick(pwm_tick),
    .PWM(PWM)
);

// Clock generation
always begin
    #5 clk = ~clk; // Toggle clock every 5 time units
end

// Stand in for the prescaler: pulse pwm_tick high for one cycle
// out of every 4 clock cycles
logic [1:0] tick_count;

always_ff @(posedge clk) begin
    tick_count <= tick_count + 1;
end

assign pwm_tick = (tick_count == 2'd3);

// Test procedure
initial begin
```

```
        $dumpfile("tb_pwm_controller.vcd");
        $dumpvars(0, tb_pwm_controller);

        clk = 0;
        rst = 1;
        tick_count = 0;
        SW = 2'b00;
        #10;
        rst = 0;

        // Run two full 64-cycle periods (1280 time units) at each duty cycle
        SW = 2'b00; #1280;   // 0 %
        SW = 2'b01; #1280;   // 12.5 %
        SW = 2'b10; #1280;   // 25 %
        SW = 2'b11; #1280;   // 50 %

        $finish;
    end

    // Log every PWM transition, so you can measure how long it stays
    // high relative to the 16-cycle period for each SW value
    always @(PWM) begin
        $display("t=%0t SW=%b PWM=%b", $time, SW, PWM);
    end

endmodule
```

Both testbenches call `$dumpfile`/`$dumpvars` up front, so running them through `anvil test` or `iverilog`/`vvp` produces a `.vcd` file you can open with `gtkwave tb_prescaler.vcd &` or `gtkwave tb_pwm_controller.vcd &`, as described earlier in this chapter. Watching `pwm_tick` and the internal counters directly in the waveform is often faster than reading through `$display` output.

4.4.5. Pin mapping

Connect the `clock` signal to the system clock (100 MHz), the `reset` signal to the middle button, switches `SW[5:0]` to the duty-cycle inputs (two bits per color), switches `SW[7:6]` to the oscilloscope channel select, the three `RGB[2:0]` outputs to the RGB LED, and `pwm_out` to a Pmod header pin for the scope probe. Add these to the project's `.xdc` file, following the same `set_property PACKAGE_PIN` / `set_property IOSTANDARD` pattern used in the tools intro:

```
## Clock signal
set_property PACKAGE_PIN E3 [get_ports {clock}]
set_property IOSTANDARD LVCMOS33 [get_ports {clock}]
create_clock -period 10.0 [get_ports {clock}]

## Switches
set_property PACKAGE_PIN J15 [get_ports {SW[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[0]}]

set_property PACKAGE_PIN L16 [get_ports {SW[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[1]}]

set_property PACKAGE_PIN M13 [get_ports {SW[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[2]}]

set_property PACKAGE_PIN R15 [get_ports {SW[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[3]}]

set_property PACKAGE_PIN R17 [get_ports {SW[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[4]}]

set_property PACKAGE_PIN T18 [get_ports {SW[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[5]}]
```

```
set_property PACKAGE_PIN U18 [get_ports {SW[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[6]}]

set_property PACKAGE_PIN R13 [get_ports {SW[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SW[7]}]

## Buttons
set_property PACKAGE_PIN N17 [get_ports {reset}]
set_property IOSTANDARD LVCMOS33 [get_ports {reset}]

## RGB LEDs
set_property PACKAGE_PIN R12 [get_ports {RGB[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {RGB[2]}]

set_property PACKAGE_PIN M16 [get_ports {RGB[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {RGB[1]}]

set_property PACKAGE_PIN N15 [get_ports {RGB[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {RGB[0]}]

## Pmod Header JA, oscilloscope probe
set_property PACKAGE_PIN C17 [get_ports {pwm_out}]
set_property IOSTANDARD LVCMOS33 [get_ports {pwm_out}]
```

4.5. Starter files

- rgb_controller_draft.sv
- rgb_controller_tb.sv

5. Fifth exercise: Counter and seven segment display

5.1. Seven segment display

A seven-segment display is an electronic display device used to show decimal digits and some letters. It consists of seven bar-shaped LEDs arranged in a figure eight. Each LED is called a segment because, when lit, it forms one part of the character being displayed. Most displays also include an eighth LED, the decimal point (DP), in the lower right corner.

As Figure 5.1 shows, segment A sits at the top and the labels run clockwise through B, C, D, E and F. Segment G is the middle bar. Lighting different combinations of segments produces the digits 0 to 9 and the hexadecimal letters A to F. For example, the digit 1 lights only B and C, while the digit 8 lights all seven segments.

5.1.1. Common anode vs common cathode configuration

Each segment is an LED, and an LED lights up only when current flows from its anode (positive terminal) to its cathode (negative terminal). To save pins, the eight LEDs of one digit share a common terminal. Which terminal they share determines the logic level that turns a segment on.

- **Common anode (CA).** All anodes are tied together and held at logic 1. Each cathode has its own control signal. Driving a cathode

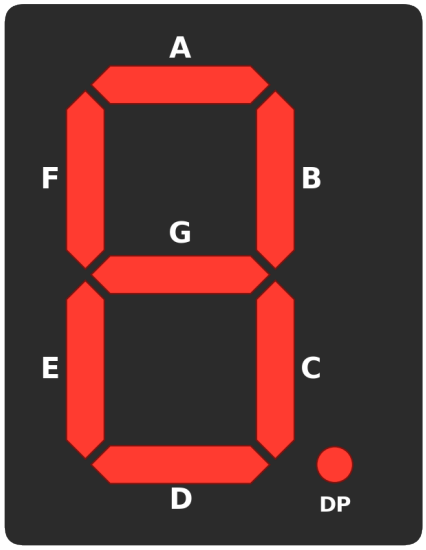


Figure 5.1.: Segment layout of a seven-segment display. Segments are labeled A to G clockwise from the top, with G in the middle. DP is the decimal point.

to logic 0 lets current flow, so the segment lights. Driving it to logic 1 leaves both terminals at the same level, so the segment stays dark. The segments are therefore **active low**.

- **Common cathode (CC).** All cathodes are tied together and held at logic 0. Each anode has its own control signal. Driving an anode to logic 1 lights the segment, and driving it to logic 0 turns it off. The segments are therefore **active high**.

Configuration	Common terminal	Segment on	Segment off
Common anode (CA)	Anodes at logic 1	Cathode at logic 0	Cathode at logic 1
Common cathode (CC)	Cathodes at logic 0	Anode at logic 1	Anode at logic 0

The Nexys A7 uses common anode displays. Keep this in mind when you write the segment patterns: a segment that should be lit needs a 0 in your code, not a 1.

5.1.2. Nexys A7 and seven-segment display

The Nexys A7 has eight common anode seven-segment digits. They are wired to the FPGA with two groups of signals:

- **Cathodes CA to CG (and DP).** These are shared by all eight digits. Segment CA on digit 0 is wired to segment CA on every other digit. A cathode at logic 0 lights its segment.
- **Anodes AN0 to AN7.** Each digit has its own anode signal, which switches that digit on or off. An anode at logic 0 turns its digit on.

  Note: You might expect the anode signals to be active high, since they drive the common anode. On the board, however, each ANx signal controls a transistor that switches the supply

to its digit. That transistor conducts when ANx is at logic 0. So both the anodes and the cathodes are active low. See Figure 9.1 in the Nexys A7 reference manual.

The board has only one set of cathode signals, so at any moment all enabled digits show the same pattern. To display eight different digits, the design uses **time multiplexing**. It enables one digit at a time and puts that digit's pattern on the shared cathodes. Then it moves on to the next digit, and so on in a continuous loop:

1. Set AN0 to logic 0 and all other anodes to logic 1. Drive the cathodes with the pattern for digit 0. Only digit 0 lights.
2. After a short time, set AN1 to logic 0 and the rest to logic 1. Drive the cathodes with the pattern for digit 1. Only digit 1 lights.
3. Continue the same way up to AN7, then start again at AN0.

Figure 5.2 shows the timing used in this lab. Each digit is on for a **digit period** of 2 ms, so one pass over all eight digits takes a **refresh period** of 8×2 ms $= 16$ ms. Each digit is lit only one eighth of the time. It still looks steady because of persistence of vision: when the refresh rate is above roughly 60 Hz, the eye cannot see the flicker. Here the refresh rate is 1 / 16 ms = 62.5 Hz. If the digit period is too long, the display visibly flickers. If it is too short, the digits look dim and can bleed into each other, because the LEDs do not have time to switch fully. The reference manual recommends a refresh period between 1 ms and 16 ms.

5.2. Assignment

In this assignment you will build a seconds counter on the Nexys A7. The counter value appears on all eight seven-segment digits as a hexadecimal number. Switch SW0 starts and stops counting, and the centre button BTNC resets the counter to zero.

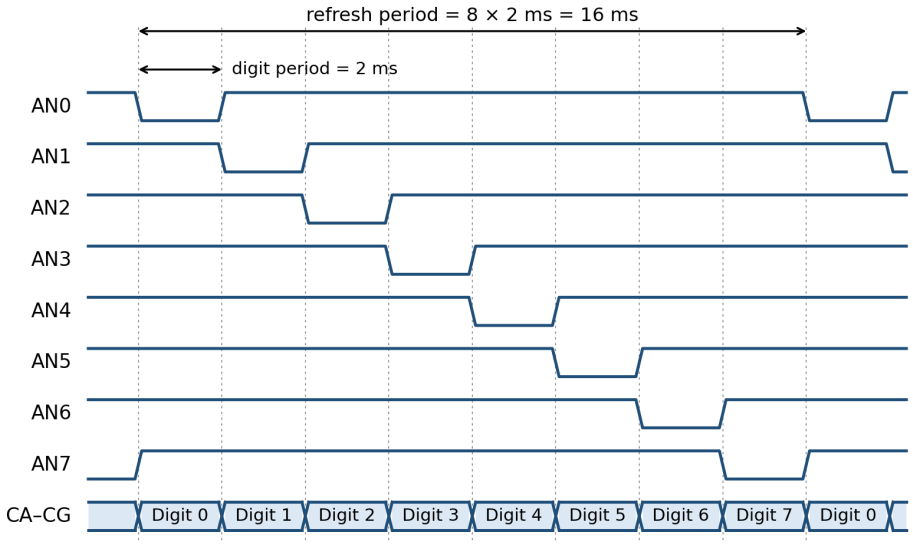


Figure 5.2.: Time multiplexing the eight digits. Exactly one anode is at logic 0 in each 2 ms slot, while the shared cathodes CA to CG carry that digit's pattern.

5.2.1. Design overview

The design has two levels of hierarchy. Figure 5.3 shows the top level. `counter_1s` produces a 32-bit count that increases once per second. `SevSegDisplay` splits that count into eight 4-bit hex digits and drives the display with time multiplexing.

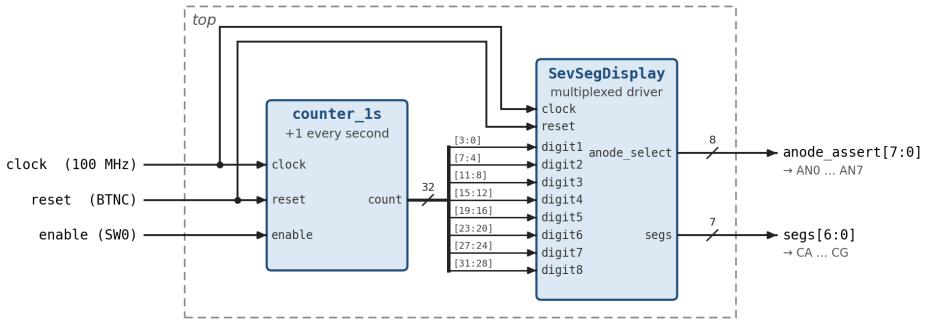


Figure 5.3.: Top-level design. The 32-bit count is split into eight nibbles, one per display digit.

Figure 5.4 shows what is inside `SevSegDisplay`. `timer_002s` produces a tick every 2 ms. On each tick, `anode_assert` moves to the next digit by driving one anode low. `value_to_digit` uses the same anode pattern to pick the matching nibble of the count. `digit_to_segments` turns that nibble into the cathode pattern.

Build the design bottom up. Write each small module first and check it in simulation, then connect the modules together. All module skeletons are in the starter file top_draft.sv.

5.2.2. Step 1: Create the project

Create a new Anvil project for the Nexys A7 100T, as in the tools intro:

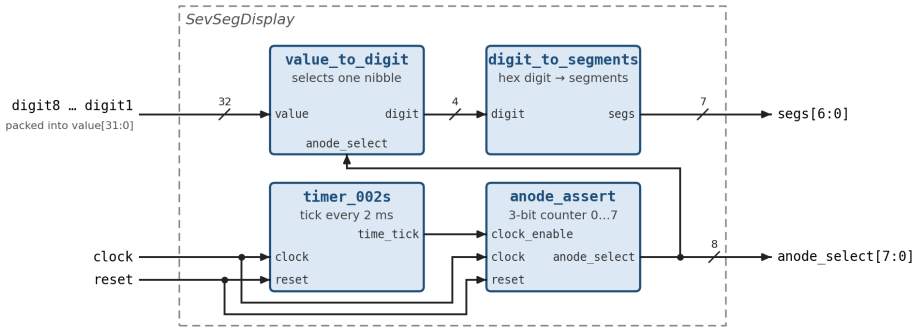


Figure 5.4.: Inside SevSegDisplay. The anode pattern from anode_assert both drives the display and selects which nibble is shown.

```
mkdir counter_7seg && cd counter_7seg
anvil init --board Nexys-A7-100T
```

Replace the contents of `top.sv` with the contents of top_draft.sv. It contains empty skeletons of every module in this assignment. You will fill them in during the following steps.

5.2.3. Step 2: `timer_002s`

This module produces a `time_tick` pulse that is high for exactly one clock cycle every 2 ms. It sets the digit period from Figure 5.2.

```
module timer_002s
    (
        input logic clock,
        input logic reset,
        output logic time_tick
```

```
    );
endmodule
```

1. Work out how many clock cycles fit in 2 ms. The clock runs at 100 MHz, so one cycle is 10 ns and 2 ms is 2 ms / 10 ns = 200 000 cycles.
2. Declare a counter register wide enough to hold 199 999. That needs 18 bits, because 2^18 = 262 144.
3. In an `always_ff` block, reset the counter to 0 when `reset` is high. Otherwise, increment it on every clock edge. When it reaches 199 999, wrap it back to 0.
4. Drive `time_tick` high only while the counter equals 199 999. This gives one pulse per 200 000 cycles.

This is the same idea as the prescaler from the previous exercise. A good alternative is to write one parametrized timer, `timer #(parameter LIMIT = 200_000)`, and use it in both this step and the next. That also makes simulation easier, as Step 9 explains.

5.2.4. Step 3: `counter_1s`

This module holds the 32-bit count. The count increases by one every second while `enable` is high, and holds its value while `enable` is low.

```
module counter_1s
    (
        input logic clock,
        input logic reset,
        input logic enable,
        output logic [31:0] count
    );
endmodule
```

1. Inside the module, build a 1 s tick in the same way as in Step 2. One second is 100 000 000 cycles, so the prescaler counts from 0 to 99 999 999. That needs 27 bits.
2. Add a second register for `count`. Reset it to 0 when `reset` is high.
3. Increment `count` only on clock cycles where the 1 s tick is high **and** `enable` is high. On all other cycles, keep the old value.

Increment `count` on the system clock and use the tick as a condition. Do not use the tick as a clock. All flip-flops in the design should share the 100 MHz clock.

5.2.5. Step 4: `anode_assert`

This module selects which digit is active. It has a 3-bit counter that advances on every 2 ms tick and turns the counter value into an active-low anode pattern.

```
module anode_assert (
    input logic clock,
    input logic reset,
    input logic clock_enable,       // time_tick from timer_002s
    output logic [7:0] anode_select
);
    logic [2:0] count;
    assign anode_select = ~(8'b1 << count);
endmodule
```

1. Write an `always_ff` block that resets `count` to 0 and increments it whenever `clock_enable` is high. A 3-bit counter wraps from 7 back to 0 on its own, so no extra comparison is needed.
2. The `assign` line is already given. Shifting `1` left by `count` sets exactly one bit, and the `~` inverts it so that exactly one anode is at logic 0:

count	anode_select	Active digit
0	8'b1111_1110 (8'hFE)	AN0, rightmost
1	8'b1111_1101 (8'hFD)	AN1
2	8'b1111_1011 (8'hFB)	AN2
…	…	…
7	8'b0111_1111 (8'h7F)	AN7, leftmost

5.2.6. Step 5: `value_to_digit`

This purely combinational module picks the nibble of the 32-bit value that belongs to the active digit.

```
module value_to_digit(
    input logic [31:0] value,
    input logic [7:0] anode_select,
    output logic [3:0] digit
);
endmodule
```

1. Write an `always_comb` block with a `case` statement on `anode_select`.
2. Add one branch per row of the table in Step 4. For `8'hFE` output `value[3:0]`, for `8'hFD` output `value[7:4]`, and so on up to `8'h7F`, which outputs `value[31:28]`.
3. Add a `default` branch that outputs `4'h0`. Without it, synthesis infers a latch.

5.2.7. Step 6: `digit_to_segments`

This purely combinational module converts a 4-bit hex digit into the seven cathode signals. Two rules from the introduction apply here:

- The bit order is `segs[6:0] = {G, F, E, D, C, B, A}`. So `segs[0]` drives segment A and `segs[6]` drives segment G (see Figure 5.1).
- The cathodes are active low. A segment that should light needs a **0**.

```
module digit_to_segments (
    input logic [3:0] digit,
    output logic [6:0] segs
);
endmodule
```

1. For each hex digit, list the segments that must light. The table below gives them.
2. Write the 7-bit pattern in the order G F E D C B A. Put a 0 for every lit segment and a 1 for every dark one.
3. Implement the table as a `case` statement inside `always_comb`, with one branch per digit.

As a worked example, take the digit 2. It lights A, B, D, E and G, and leaves C and F dark. Reading G F E D C B A gives 0 1 0 0 1 0 0, so `segs = 7'b0100100`.

Digit	Lit segments	`segs` (G…A)
0	A B C D E F	`7'b1000000`
1	B C	`7'b1111001`
2	A B D E G	`7'b0100100`
3	A B C D G	
4	B C F G	
5	A C D F G	
6	A C D E F G	
7	A B C	
8	A B C D E F G	
9	A B C D F G	
A	A B C E F G	
b	C D E F G	

Digit	Lit segments	`segs` (G…A)
C	A D E F	
d	B C D E G	
E	A D E F G	
F	A E F G	

Fill in the missing patterns yourself. Lowercase b and d are used so they do not look like 8 and 0.

5.2.8. Step 7: `SevSegDisplay`

Now connect the four modules as shown in Figure 5.4.

```
module SevSegDisplay (
    input logic clock,
    input logic reset,
    input logic [3:0] digit1, // least significant digit, shown on AN0
    input logic [3:0] digit2,
    input logic [3:0] digit3,
    input logic [3:0] digit4,
    input logic [3:0] digit5,
    input logic [3:0] digit6,
    input logic [3:0] digit7,
    input logic [3:0] digit8, // most significant digit, shown on AN7
    output logic [7:0] anode_select,
    output logic [6:0] segs
);
    logic [31:0] digit;
    assign digit = {digit8, digit7, digit6, digit5, digit4, digit3, digit2, d
endmodule
```

1. Declare two internal signals: `logic time_tick` and `logic [3:0] current_digit`. Do not name the 4-bit signal `digit`, because the skeleton already uses `digit` for the packed 32-bit value.
2. Instantiate `timer_002s`. Connect `clock` and `reset`, and connect its output to `time_tick`.
3. Instantiate `anode_assert`. Connect `clock`, `reset` and `.clock_enable(time_tick)`. Connect its output straight to the module output `anode_select`.
4. Instantiate `value_to_digit` with `.value(digit)`, `.anode_select(anode_select)` and `.digit(current_digit)`. This is the feedback path in the figure. The same anode pattern that drives the display also selects the nibble.
5. Instantiate `digit_to_segments` with `.digit(current_digit)` and connect its output to the module output `segs`.

5.2.9. Step 8: `top`

The top module connects the counter to the display, as shown in Figure 5.3.

```
module top (
    input logic clock,
    input logic reset,
    input logic enable,
    output logic [7:0] anode_assert,
    output logic [6:0] segs
);
endmodule
```

1. Declare an internal signal `logic [31:0] count`.
2. Instantiate `counter_1s` and connect `clock`, `reset`, `enable` and `count`.

3. Instantiate `SevSegDisplay`. Connect `clock` and `reset`. Then connect the eight nibbles of `count`: `.digit1(count[3:0])`, `.digit2(count[7:4])`, and so on up to `.digit8(count[31:28])`.
4. Connect `.anode_select(anode_assert)` and `.segs(segs)` to the top-level outputs.

5.2.10. Step 9: Simulate

Simulate before you build. Finding a bug in GTKWave takes minutes. Finding it on the board takes much longer.

With the real limits, one second of hardware time is 100 million clock cycles, which is far too slow to simulate. Temporarily shrink the limits instead. For example, make the 2 ms timer tick every 4 cycles and the 1 s timer every 64 cycles. A parametrized timer from Step 2 makes this a one-line change. Remember to restore the real values before you build.

Use top_tb.sv as a starting point. Put it in the project's `tb/` folder and run it:

```
anvil test tb/top_tb.sv
gtkwave tb/top_tb.vcd &
```

In the waveform, check that:

- `anode_assert` steps through `FE`, `FD`, `FB`, … `7F` and then starts again at `FE`.
- `segs` shows the correct pattern for the nibble selected by each anode value.
- `count` increases only while `enable` is high, and returns to 0 when `reset` is pressed.

It also helps to test `digit_to_segments` on its own with a small testbench that loops through all 16 digits.

5.2.11. Step 10: Pin constraints

Map the top-level ports to the board pins in the project's `.xdc` file, following the same pattern as in the tools intro. The clock is the 100 MHz oscillator, `enable` is SW0, `reset` is BTNC, and the outputs go to the seven-segment cathodes and anodes:

```
## Clock signal
set_property PACKAGE_PIN E3 [get_ports {clock}]
set_property IOSTANDARD LVCMOS33 [get_ports {clock}]
create_clock -period 10.0 [get_ports {clock}]

## Switch SW0
set_property PACKAGE_PIN J15 [get_ports {enable}]
set_property IOSTANDARD LVCMOS33 [get_ports {enable}]

## Button BTNC
set_property PACKAGE_PIN N17 [get_ports {reset}]
set_property IOSTANDARD LVCMOS33 [get_ports {reset}]

## Seven-segment cathodes CA to CG
set_property PACKAGE_PIN T10 [get_ports {segs[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[0]}]
set_property PACKAGE_PIN R10 [get_ports {segs[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[1]}]
set_property PACKAGE_PIN K16 [get_ports {segs[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[2]}]
set_property PACKAGE_PIN K13 [get_ports {segs[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[3]}]
set_property PACKAGE_PIN P15 [get_ports {segs[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[4]}]
set_property PACKAGE_PIN T11 [get_ports {segs[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[5]}]
```

```
set_property PACKAGE_PIN L18 [get_ports {segs[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {segs[6]}]

## Seven-segment anodes AN0 to AN7
set_property PACKAGE_PIN J17 [get_ports {anode_assert[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[0]}]
set_property PACKAGE_PIN J18 [get_ports {anode_assert[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[1]}]
set_property PACKAGE_PIN T9 [get_ports {anode_assert[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[2]}]
set_property PACKAGE_PIN J14 [get_ports {anode_assert[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[3]}]
set_property PACKAGE_PIN P14 [get_ports {anode_assert[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[4]}]
set_property PACKAGE_PIN T14 [get_ports {anode_assert[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[5]}]
set_property PACKAGE_PIN K2 [get_ports {anode_assert[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[6]}]
set_property PACKAGE_PIN U13 [get_ports {anode_assert[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_assert[7]}]
```

The decimal point (DP, pin H15) is not used in this design. If you leave it unconnected, it stays dark.

5.2.12. Step 11: Build and program

Check that the timer limits are back at their real values (200 000 and 100 000 000). Then build and program the board:

```
anvil build
anvil program
```

All eight digits should show `00000000`. Turn on SW0, and the rightmost digit should count up once per second: 1, 2, … 9, A, b, … F. Then the next digit increments to 1. Turning SW0 off freezes the value, and pressing BTNC clears it to zero.

If the display looks wrong, use these hints:

- **All segments lit, or the digits look like garbled 8s:** the segment patterns are probably inverted. Remember that a lit segment needs a 0.
- **The same digit appears on every position:** check the `case` in `value_to_digit` and the connection from `anode_select` to it.
- **The digits flicker visibly:** the 2 ms timer is too slow. Check the limit in `timer_002s`.

5.3. Starter files

- top_draft.sv
- top_tb.sv

Part II.

Appendix

6. Appendix: Using the Oscilloscope and Signal Generator

This appendix covers the two pieces of lab equipment you will connect to the FPGA board whenever an exercise asks you to probe a signal directly, starting with the oscilloscope extension in the PWM RGB exercise. The same equipment and the same Pmod probing convention come back again in the SoC verification lab later in the course.

6.1. Equipment

- **Oscilloscope**: Rigol DHO914, a digital oscilloscope used to capture and analyze electrical signals in real time.
- **Signal generator**: Rigol DG912 Pro, used wherever an exercise asks you to compare a signal from the board against a known reference waveform.

Simulation only shows how a design behaves in an idealized model. Real hardware adds effects simulation cannot show you: clock jitter, I/O delays, signal integrity issues, and interaction with external peripherals. Measurement equipment lets you check timing, frequency, and duty cycle against the actual signal coming off the board, not just the one your testbench predicts.

> **Power-on order**
>
> Turn the equipment on in this order: oscilloscope first, then the signal generator, then the FPGA board. Powering them on in a different order risks damaging the equipment.

6.2. Connecting probes to the FPGA board

Several exercises route the signal to observe out through the JA Pmod header, using pin 1 as the signal and pin 5 as ground. The pinout is:

- Connect the oscilloscope probe's ground clip to the GND pin (pin 5) of the JA Pmod header.
- Connect the probe tip to the signal pin (pin 1) of the JA Pmod header, for example the `pwm_out` signal from the PWM RGB exercise.
- Also connect the FPGA board's ground to the oscilloscope's ground, so both share a common reference point.

Set the probe's attenuation switch to 1X. A 10X setting attenuates the signal before it reaches the oscilloscope and will distort your reading.

If an exercise also asks you to compare against a reference signal from the signal generator, connect the generator's output (CH1) to the oscilloscope's second channel (CH2) with a BNC cable.

6.3. Using the Rigol DHO914 oscilloscope

When you power on the oscilloscope, the main screen displays the waveforms captured on each channel.

The yellow box next to the RIGOL logo in the lower left corner shows which channel is currently selected, CH1 in the image above. Press a channel's button on the front panel to select it. Each channel has its own vertical scale, coupling, and position settings.

6.3.1. Adjusting the display

The waveform grid's horizontal axis is time, the vertical axis is voltage.

- The **Sec/DIV** knob sets the time scale, how much time one horizontal grid division represents.
- Each channel's **Volts/DIV** knob sets that channel's voltage scale, how much voltage one vertical grid division represents.
- Each channel's **Position** knob, and the **Horizontal Position** knob, move the waveform on screen without changing its scale. Use them to center a waveform for a closer look.
- The **Auto** button automatically picks scale and position settings for whatever signal is connected. It's a good starting point when you aren't yet sure what the signal looks like.
- The **Run/Stop** button freezes the current acquisition. Press it again to resume capturing.

6.3.2. Measuring signal parameters

Press the **Measure** button (or the Measure knob, to the left of the Auto button) to open the measurement menu.

Measurements are grouped into three categories:

- **Vertical**: voltage-related measurements such as Vmax, Vmin, Vavg, Vpp, and Vrms.

- **Time**: time-related measurements such as Frequency, Period, Rise Time, Fall Time, and Duty Cycle.
- **Other**: delay, phase, and similar cross-channel measurements.

Select the parameters relevant to what you're verifying. For a PWM signal that is usually Period, Freq, and +Duty.

Close the measurement menu once you've made your selections. The chosen measurements stay on screen on the right side of the waveform display and update live as the oscilloscope keeps capturing.

6.4. Using the DG912 Pro signal generator

The DG912 Pro outputs sine, square, triangle, pulse, noise, DC, and arbitrary waveforms through two channels, CH1 and CH2. Most exercises only need CH1.

For each channel you can set:

- **Waveform type**: square, sine, triangle, ramp, pulse, noise, DC, or arbitrary.
- **Frequency**: press **FREQ**, enter the value on the numeric keypad, and confirm with **ENTER**.
- **Amplitude**: press **VPP** to set the peak-to-peak voltage, or **OFFSET** to set the DC offset the waveform is centered around. An offset of 0V means the waveform swings between +VPP/2 and -VPP/2. The **Ampl/HighL** button switches between VPP/offset and high/low voltage level entry, whichever is more convenient for the levels you need.
- **Duty cycle** (square waves): press **DUTY**, enter a percentage from 0 to 100, and confirm with **ENTER**. Duty cycle is the fraction of one period the signal spends high. 50% means high for half the period and low for the other half.

- **Phase**: press **PHASE** and enter a value in degrees from 0 to 360, the shift of the waveform relative to a reference point in time.

Once configured, enable the channel's output by pressing the gray area next to it. It lights up yellow when the output is active.

> To match a 3.3V FPGA output level on a reference channel, set VPP to 3.3V and Offset to 1.65V, so the signal swings from 0V to 3.3V instead of being centered on 0V.